

ASSIGNMENT -1

SUBHASHRI K S (111519106154)

Please create circuit with Piezo alarm, PIR sensor, tmp sensor with below functionalities:

1. Alarm should sound in one manner if temp is above 60 C
2. Alarm should sound with another frequency if motion is detected in PIR sensor.

